
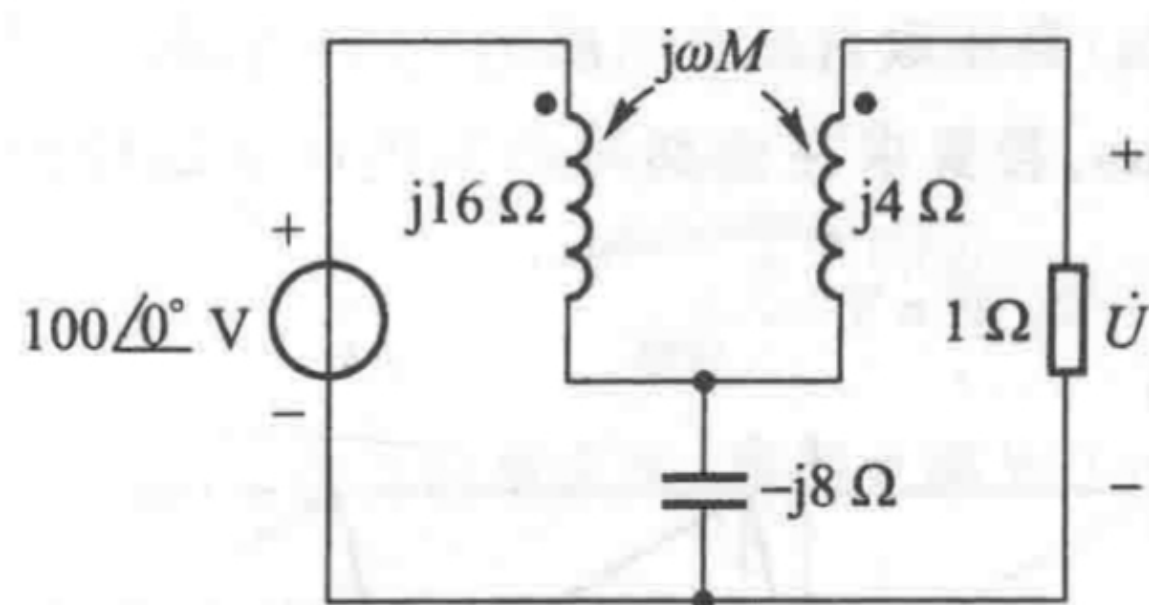


# 第十一章作业

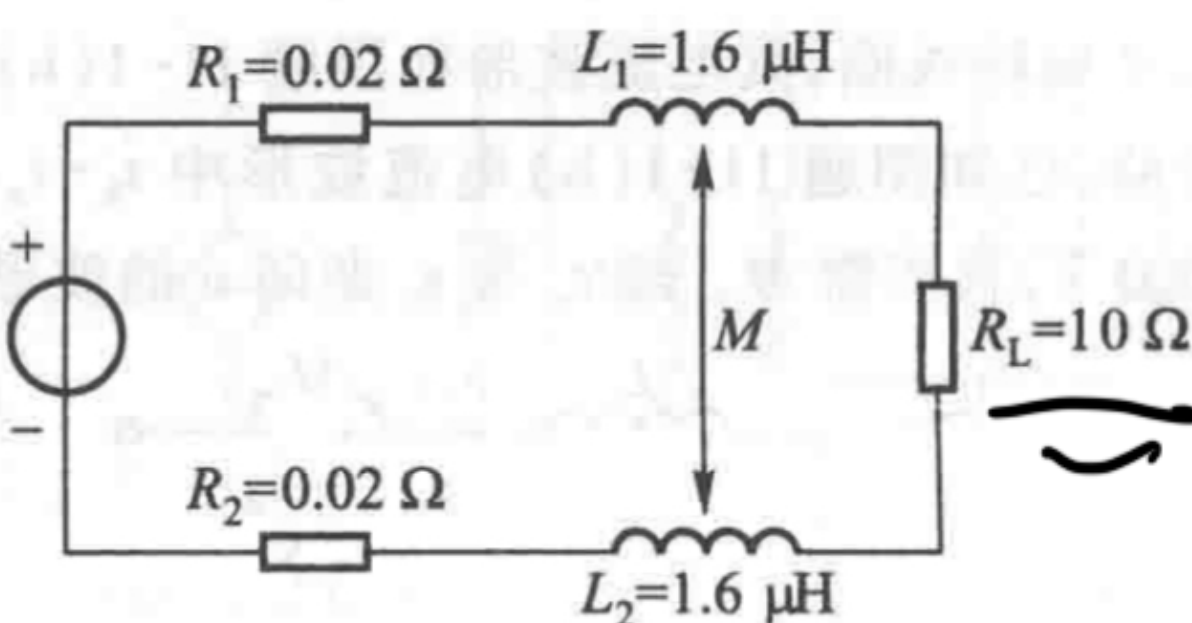


图题 11-4



图题 11-5

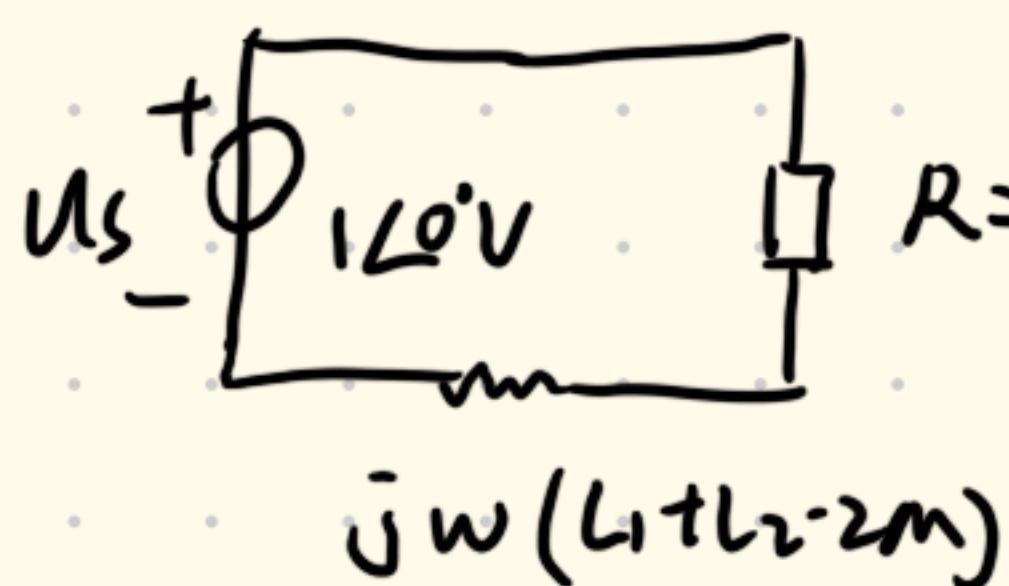11-5 同轴电缆的外导体与内导体之间总存在一些互感,图题 11-5 所示电缆用来传送 1 MHz 信号至负载  $R_L$ , 试计算耦合系数  $k$  为 0.75 和 1 时传给负载的功率。已知  $\dot{U}_s = 1\angle 0^\circ \text{ V}$ 。

$$\frac{M}{\sqrt{L_1 L_2}} = k \Rightarrow M = k\sqrt{L_1 L_2} \quad \begin{cases} \text{① } k=1 \text{ 时 } M=1.6 \mu\text{H} \\ \text{② } k=0.75 \text{ 时 } M=1.2 \mu\text{H} \end{cases}$$



①  $k=1$  时  $L_1 + L_2 - 2M = 0$

$$\therefore \dot{I} = \frac{\dot{U}}{R} = \frac{1\angle 0^\circ \text{ V}}{10.04\Omega} = 0.0996\angle 0^\circ \text{ A}$$


$$P = I^2 R_L = 99.2 \text{ mW}$$

②  $k=0.75$  时  $L = L_1 + L_2 - 2M = 0.8 \mu\text{H}$


$$\dot{I} = \frac{\dot{U}}{j\omega L + R} = \frac{1\angle 0^\circ}{j2\pi \times 10^6 \times 0.8 \times 10^{-6} + 10.04} = \frac{1\angle 0^\circ}{j1.6 + 10.04} = \frac{1\angle 0^\circ}{1.23\angle 26.59^\circ} = 0.089\angle -26.59^\circ$$

$$P = I^2 R_L = 0.089^2 \times 10 = 79.2 \text{ mW}$$

11-6 求图题 11-6 所示电路中的  $i_1$  和  $i_2$ , 已知  $u_s(t) = 100\cos(10^3 t + 30^\circ) \text{ V}$ 。

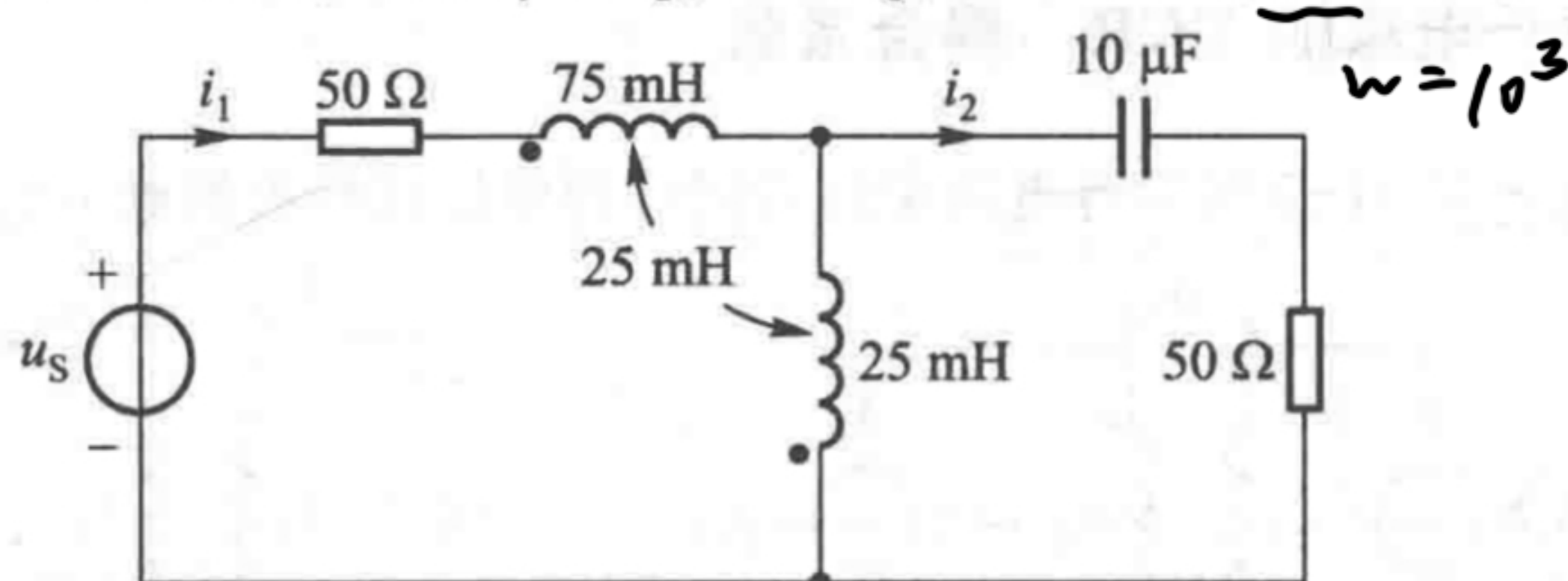

图题 11-6

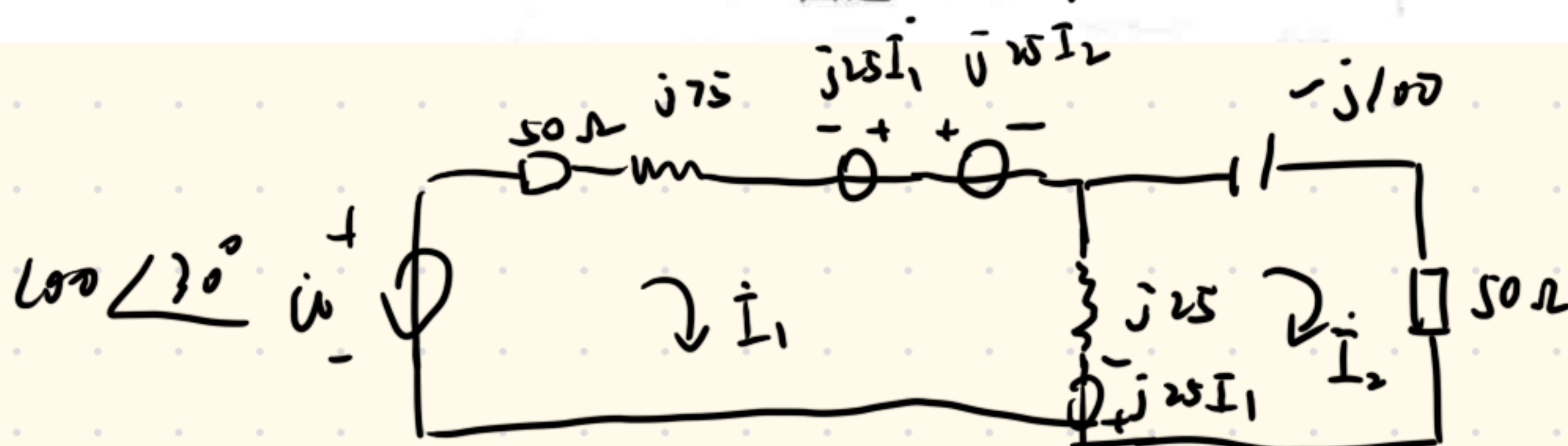




$$\begin{cases} (50 + j75)\dot{I}_1 - j15\dot{I}_1 + j15\dot{I}_2 + j15(\dot{I}_1 - \dot{I}_2) - j15\dot{I}_1 - \dot{U} = 0 \\ -j100\dot{I}_2 + 50\dot{I}_2 + j15\dot{I}_1 + j15(\dot{I}_2 - \dot{I}_1) = 0 \end{cases}$$

$$\begin{cases} (50 + j50)\dot{I}_1 - \dot{U} = 0 \\ (-j75 + 50)\dot{I}_2 = 0 \end{cases} \Rightarrow \begin{cases} \dot{I}_1 = \frac{100 \angle 30^\circ}{50 \angle 45^\circ} = \sqrt{2} \angle -15^\circ \\ \dot{I}_2 = 0 \end{cases}$$


$$\therefore i_1(t) = \sqrt{2} \cos(10^3 t - 15^\circ) \text{ A}$$

$$i_2(t) = 0 \text{ A}$$

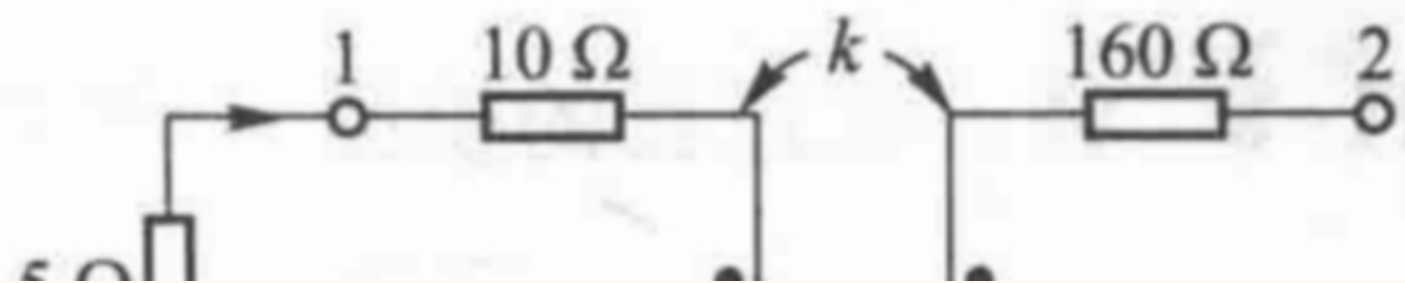11-9 已知空心变压器的参数:  $L_1 = 9 \text{ H}$ 、 $R_1 = 200 \Omega$ 、 $L_2 = 4 \text{ H}$ 、 $R_2 = 100 \Omega$  及  $k = 0.5$ 。所接负载为  $800 \Omega$  电阻和  $1 \mu\text{F}$  电容串联, 所接正弦电压源频率为  $400 \text{ rad/s}$ , 电压有效值为  $300 \text{ V}$ , 内阻为  $500 \Omega$ , 内电感为  $0.25 \text{ H}$ 。试求传送给负载的功率  $P$  和空心变压器的功率传输效率。



$$M = \sqrt{L_1 L_2} k = 3 \text{ H}$$

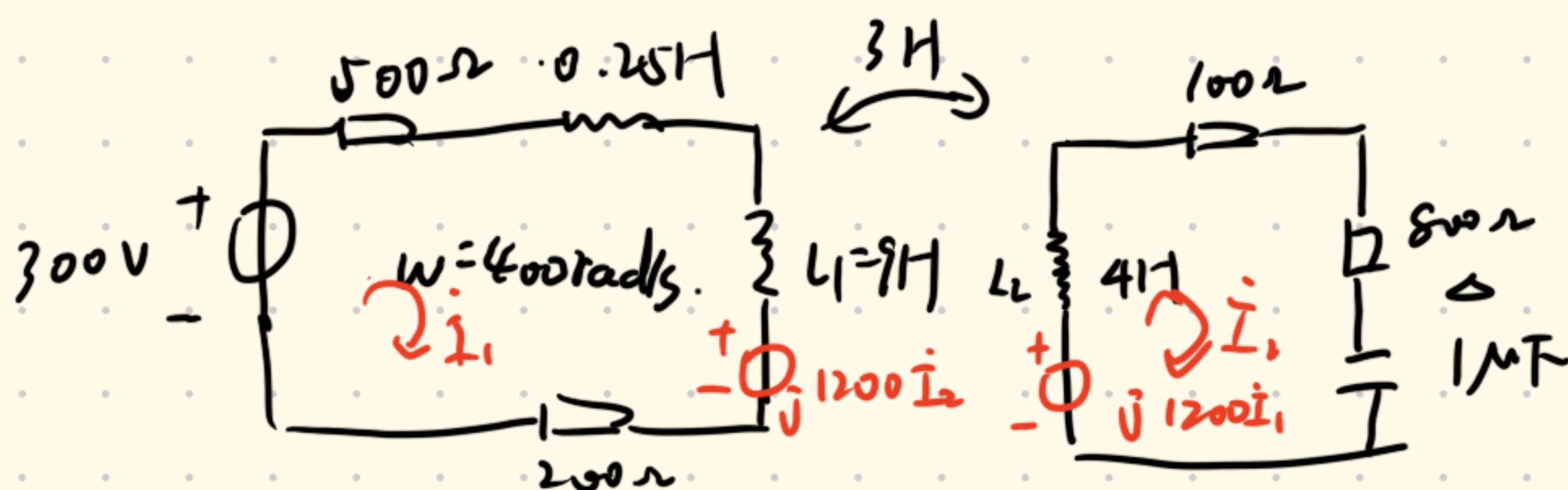

$$\begin{aligned} & -j \frac{1}{1 \times 10^{-6} \times 400} \\ & = -j \frac{1}{4} \times 10^4 \\ & = \end{aligned}$$

$$\text{网孔 } L_1: (500 + 200 + j100 + j1600)\dot{I}_1 - j1200\dot{I}_2 = 300 \angle 0^\circ$$

$$\text{网孔 } L_2: (900 + j1600 - j1500)\dot{I}_2 - j1200\dot{I}_1 = 0$$

$$\Rightarrow \begin{cases} (700 + j3700)\dot{I}_1 - j1200\dot{I}_2 = 300 \angle 0^\circ \\ (900 - j900)\dot{I}_2 - j1200\dot{I}_1 = 0 \end{cases}$$

$$37 \times 3 = 111 \quad -132 - 48$$

$$\Rightarrow \begin{cases} (7 + j37)\dot{I}_1 = 3 + j12\dot{I}_2 \\ j4\dot{I}_1 = (3 - j3)\dot{I}_2 \end{cases}$$

$$3(7 + j37)(-1 - j)\dot{I}_2 = 12 + j48\dot{I}_2$$

$$(21 + j111)(-1 - j)\dot{I}_2 - j48\dot{I}_2 = 12$$

$$(-21 + 111 - j111 - j21 - j48)\dot{I}_2 = 12$$

$$(90 - j180)\dot{I}_2 = 12$$

$$\dot{I}_1 = \frac{3 - j3}{j4}\dot{I}_2 = \frac{3}{4}(-1 - j)\dot{I}_2$$

$$\dot{I}_2 = 0.0596 \angle 63.43^\circ$$

$$\Rightarrow \frac{3(7 + j37)(-1 - j)}{4}\dot{I}_2 = 3 + j12\dot{I}_2$$

$$P_2 = (0.0596)^2 \cdot 800 \approx 2.842 \text{ W}$$




$$\dot{I}_1 = \frac{3}{4}(-j) \cdot \frac{12}{90-j180} = 0.0632 \angle -71.57^\circ$$

$$P_1 = U \dot{I}_1 \cos \theta = 300 \times 0.0632 \times \cos(-71.57^\circ) \approx 6.00 \text{ W}$$

$$\eta = \frac{P_2}{P_1} = \frac{2.842}{6 - 500 \times 0.0632^2} \approx 71\%$$

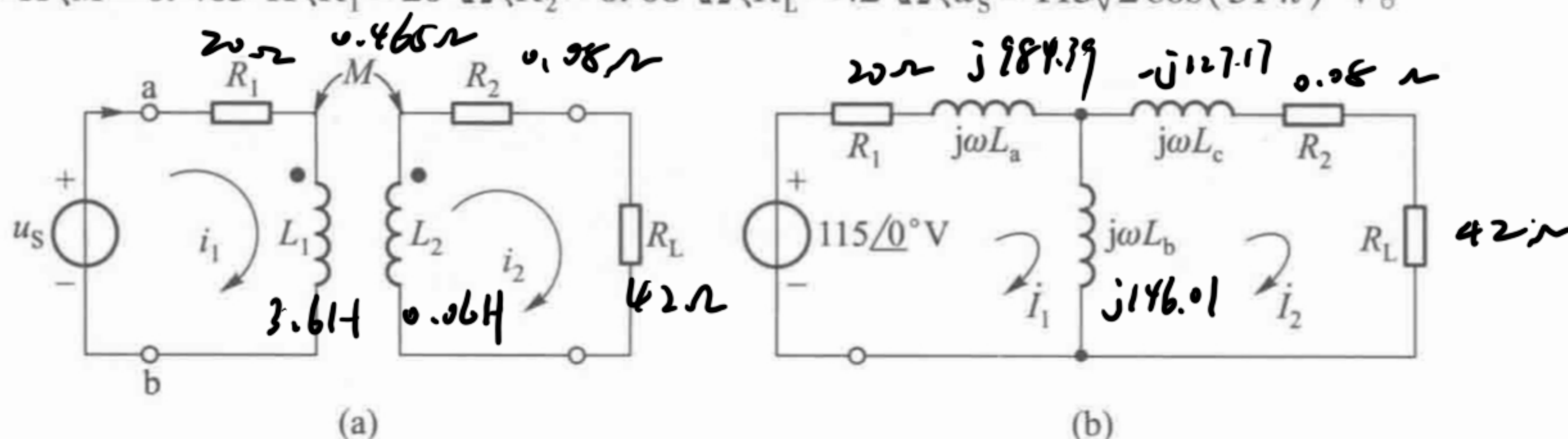11-11 试利用 T 形去耦电路求解例 11-5。

解 为方便计,特将例 11-5 电路图绘为图题解 11-11(a),其  $L_1 = 3.6 \text{ H}$ 、 $L_2 = 0.06 \text{ H}$ 、 $M = 0.465 \text{ H}$ 、 $R_1 = 20 \Omega$ 、 $R_2 = 0.08 \Omega$ 、 $R_L = 42 \Omega$ 、 $u_s = 115\sqrt{2} \cos(314t) \text{ V}$ 。



$$L_a = L_1 - M = 3.6 - 0.465 = 3.135 \text{ H}$$

$$L_c = L_2 - M = -0.405 \text{ H}$$

$$L_b = M = 0.465 \text{ H}$$


$$\text{网孔1: } (20 + j1130.4) \dot{I}_1 - j146.01 \dot{I}_2 = 115 \angle 0^\circ$$

$$\text{网孔2: } (42.08 + j18.84) \dot{I}_2 - j146.01 \dot{I}_1 = 0$$


$$(20 + j1130.4) \dot{I}_1 - j146.01 \cdot \frac{j146.01}{42.08 + j18.84} \dot{I}_1 = 115$$

$$\dot{I}_1 = 0.1106 \angle -64.85^\circ \text{ A} = 110.6 \angle -64.85^\circ \text{ mA}$$

11-13 电路如图题 11-10 所示,已知  $\dot{U} = 10 \angle 0^\circ \text{ V}$ ,试求  $\dot{U}_s$ 。

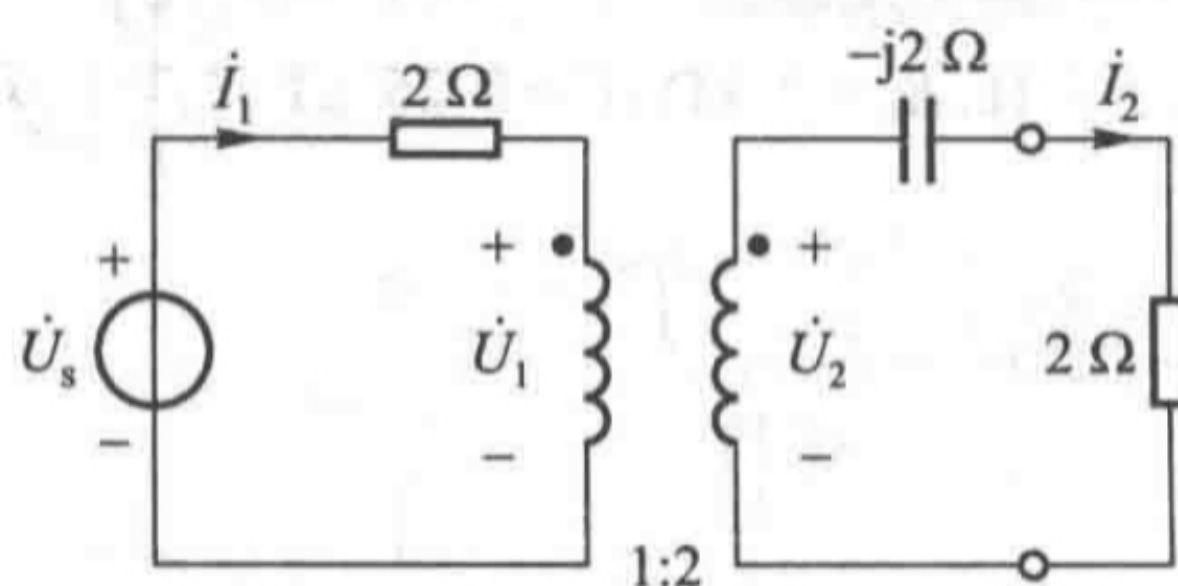

图题 11-10

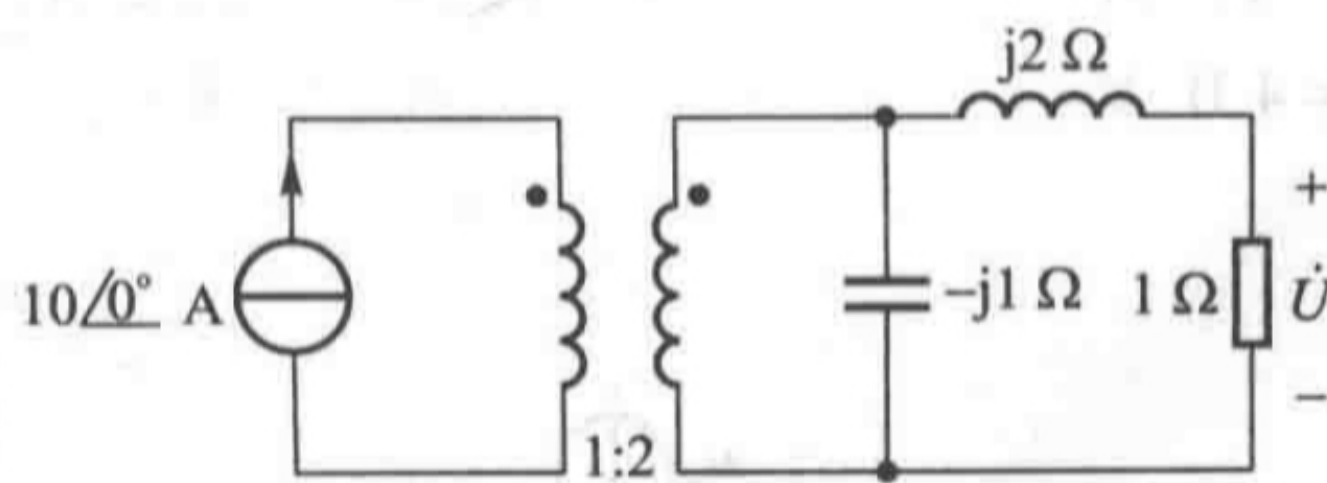

图题 11-11

$$\dot{I}_2 = \frac{\dot{U}}{2} = 5 \angle 0^\circ \text{ A}$$



$$U_c = \dot{I}_2 \cdot Z_c = 5\angle 0^\circ \cdot 2\angle -90^\circ = 10\angle -90^\circ \text{ V}$$


$$\therefore \dot{U}_2 = \dot{U}_c + \dot{U} = (10 - j10) \text{ V}$$

$$\therefore \dot{U}_1 = \frac{1}{2} \dot{U}_2 = (5 - j5) \text{ V}$$


$$\dot{I}_1 = 2\dot{I}_2 = 10\angle 0^\circ \text{ A}$$

$$\therefore \dot{U}_s = \dot{U}_1 + 2\dot{I}_1 = 20 + 5 - j5 = (25 - j5) \text{ V}$$

$$= 25.495 \angle -11.31^\circ \text{ V}$$

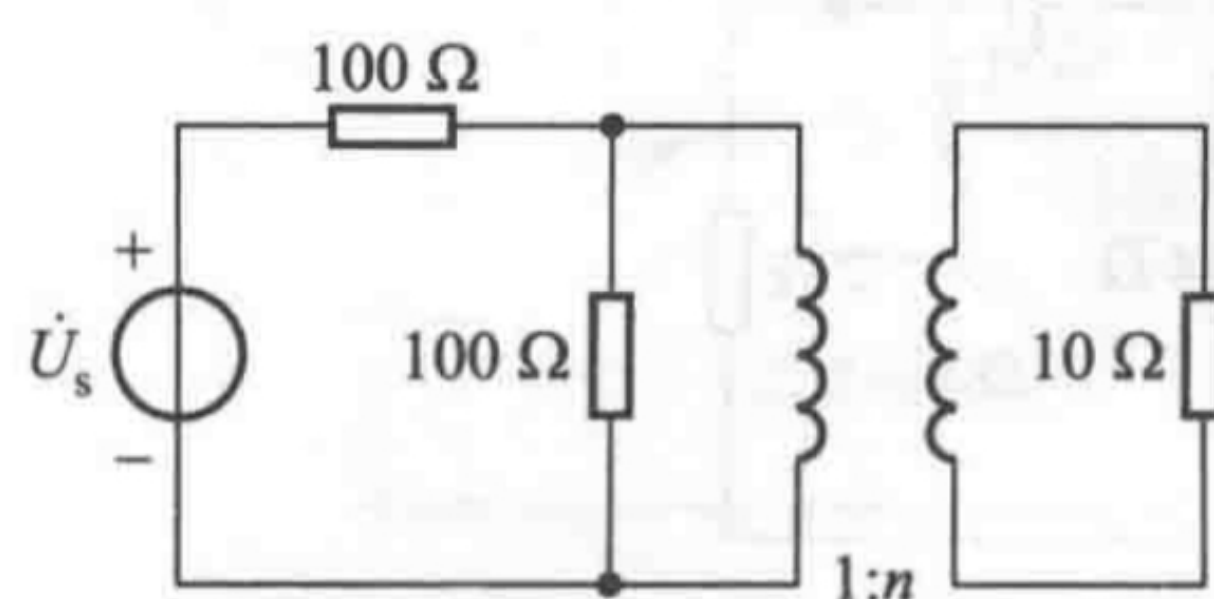

图题 11-12

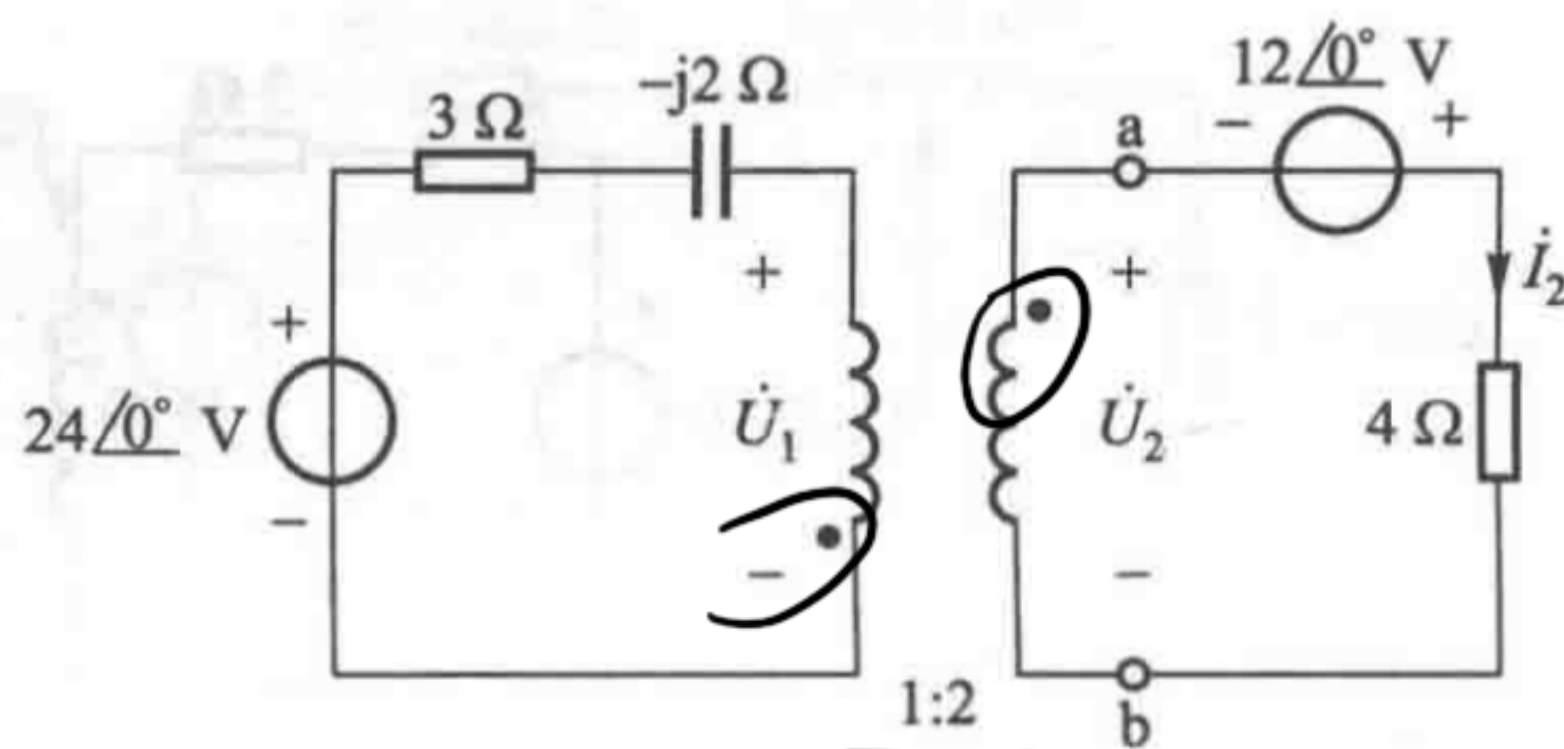


图题 11-13

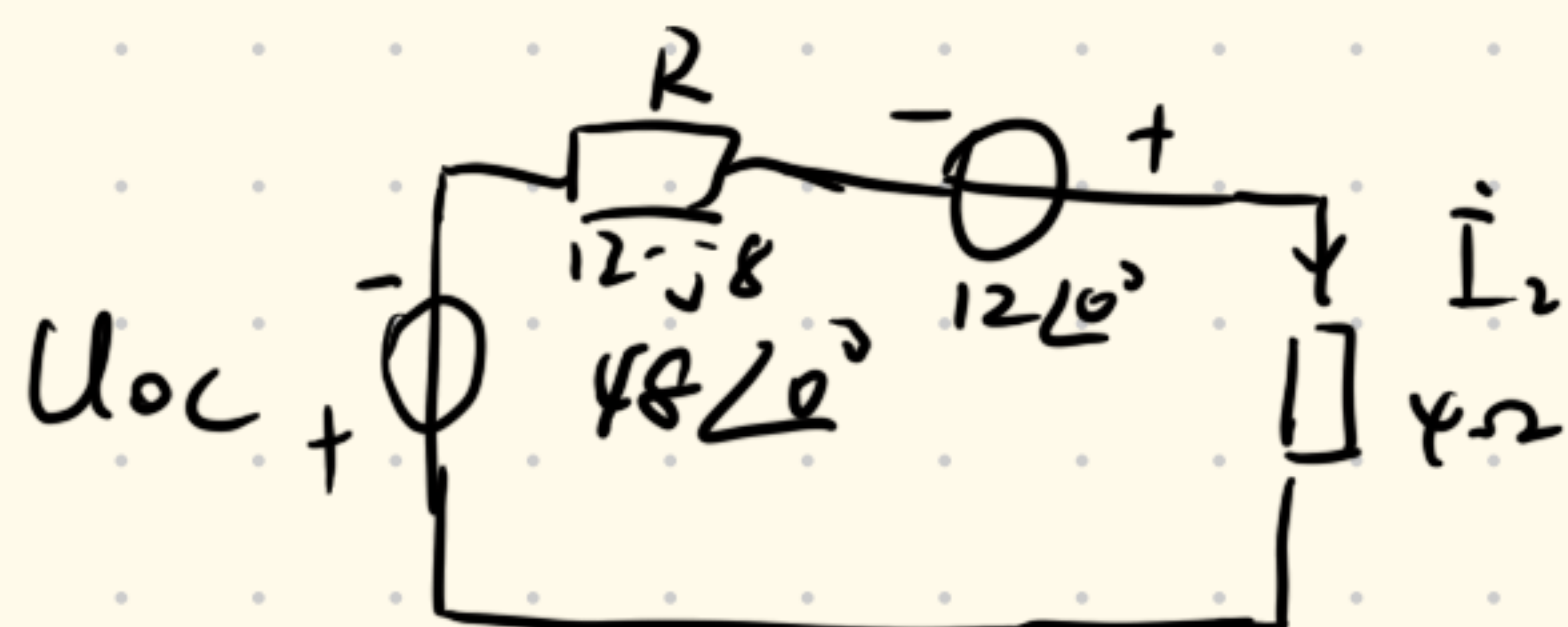11-10 电路如图题 11-13 所示, 试求 ab 左侧的戴维南等效电路, 并由此求解  $\dot{I}_2$ 。

$$R = 2^2(3 - j2) = (12 - j8) \Omega$$


$$U_{oc} = -2 \cdot 24\angle 0^\circ \text{ V} = -48\angle 0^\circ \text{ V}$$



$$(12 - j8 + 4)\dot{I}_2 - 12\angle 0^\circ + 48\angle 0^\circ = 0$$

$$\dot{I}_2 = \frac{-36\angle 0^\circ}{16 - j8} = -2.01\angle 26.57^\circ \text{ A}$$

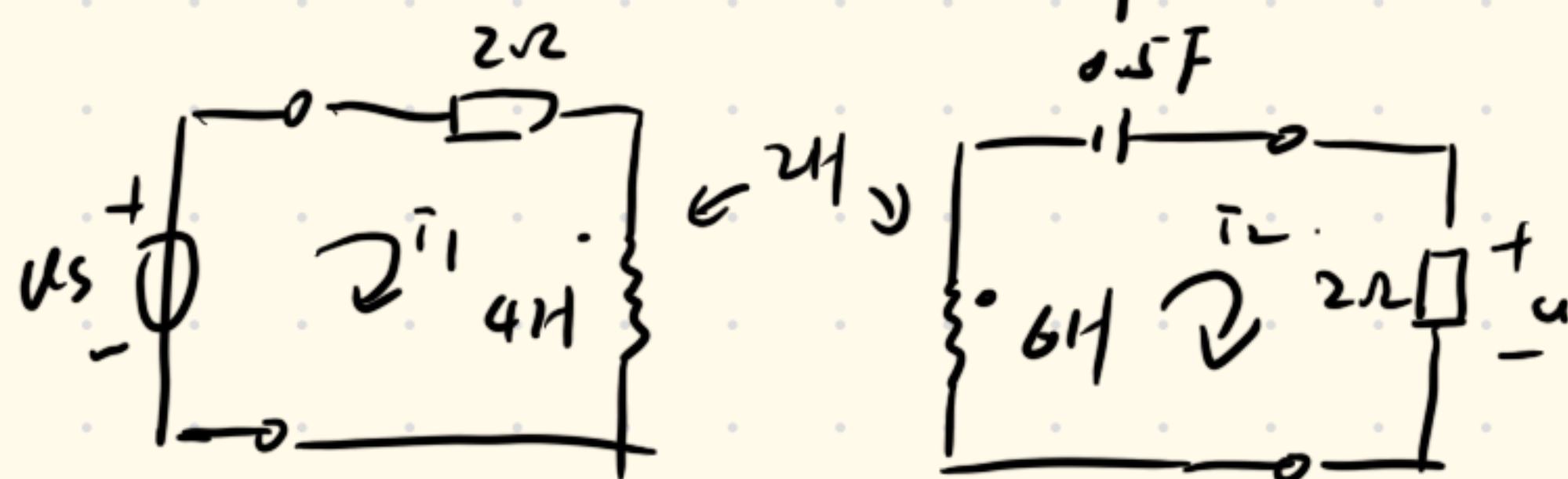11-3  $u_s = 24\cos(\omega t + 30^\circ) \text{ V}$ , 试求输出电压  $u(t)$



$$\dot{U}_{sm} = 24\angle 30^\circ$$


$$Z_1 = 2 + j4 + \frac{\omega M^2}{Z_2} = 2 + j4 + \frac{2}{1 + j2} \quad \therefore \dot{I}_{1m} = \frac{24\angle 30^\circ}{2 + j4 + \frac{2}{1 + j2}} = 6\angle 156.8^\circ \text{ A}$$



$$\dot{U}_m = \dot{I}_m \times \frac{2}{2 - j2 + j6} = 5.36 \angle 3.4^\circ \text{ V}$$

$$u(t) = 5.36 \cos(t + 3.4^\circ) \text{ V}$$

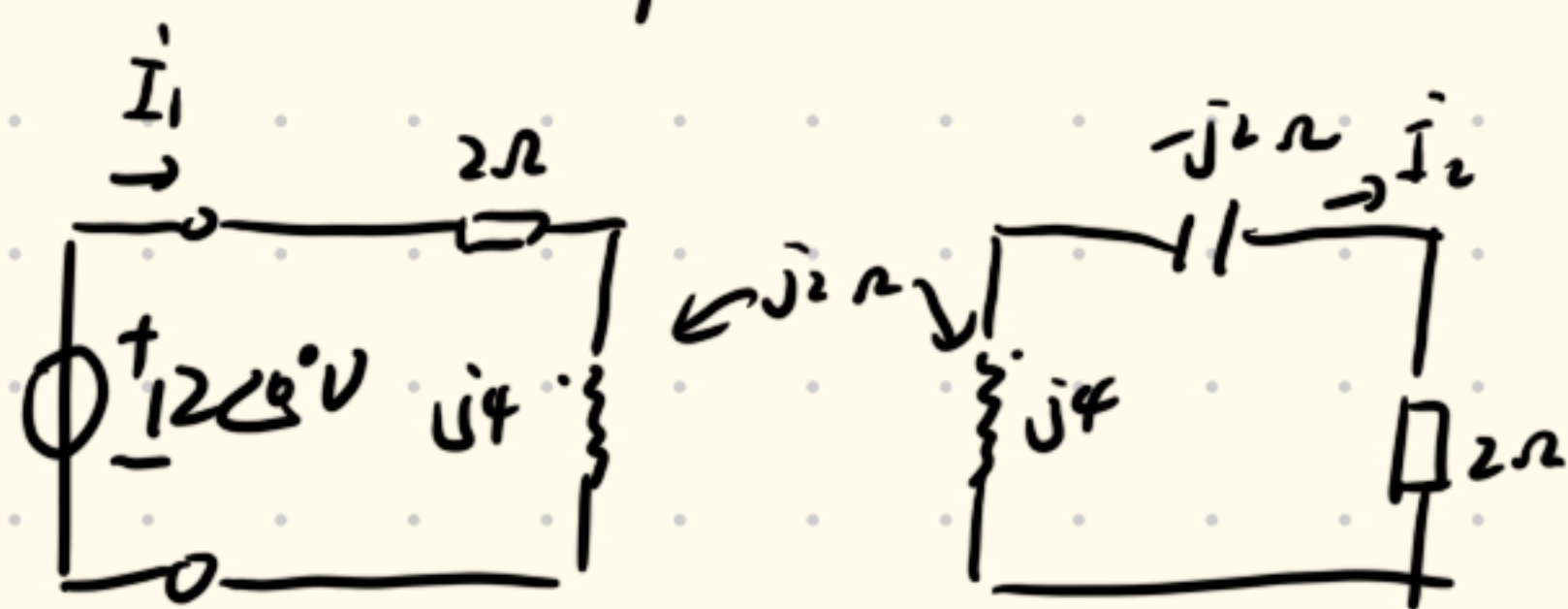11-8 求对电源端的输入阻抗, 电流  $\dot{I}_1$  和  $\dot{I}_2$




$$Z_i = \frac{2^2}{j2+2} + 2 + j4 = 3 + j3 \Omega$$

$$\dot{I}_1 = \frac{12 \angle 0^\circ}{3 + j3} = 2\sqrt{2} \angle -45^\circ \text{ A}$$

$$\dot{I}_2 = \frac{j2\dot{I}_1}{2j2 + j4} = 2 \angle 0^\circ \text{ A}$$

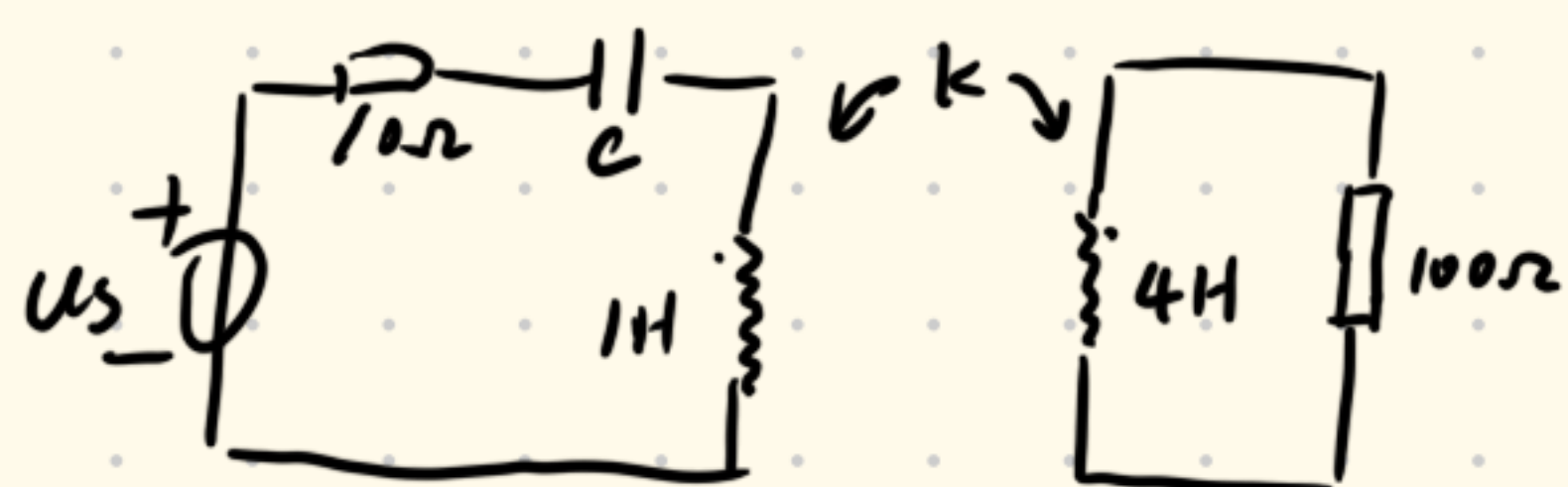11-21  $\omega = 1000 \text{ rad/s}$  串联谐振. 试求  $C$ , 已知  $k = 0.5$ .



$$M = k\sqrt{L_1 L_2} = 0.5\sqrt{4} = 1 \text{ H}$$

$$Z_{\text{ref}} = \frac{\omega^2 M^2}{Z_{22}} = \frac{10^6}{100 + j4000} = 6.25 - j249.8 \Omega$$

$$Z_{\text{in}} = Z_{11} + Z_{\text{ref}} = 10 - j\frac{1}{1000C} + j1000 + 6.25 - j249.8$$

$$\text{虚部为零} \Rightarrow -\frac{1}{1000C} + 1000 - 249.8 = 0 \Rightarrow C = 1.33 \mu\text{F}$$